

1.  $001 \rightarrow 011 \rightarrow 010 \rightarrow 110 \rightarrow 111 \rightarrow 101 \rightarrow 100$  <sup>5</sup>

(1) Truth table

CBA	$C^+$	$B^+$	$A^+$
000	X	X	X
001	0	1	1
010	1	1	0
011	0	1	0
100	0	0	1
101	1	0	0
110	1	1	1
111	1	0	1

$C^+$		$B^+$		$A^+$	
BA	C	BA	C	BA	C
00	0 1	00	0 1	00	0 1
01	X 0	01	X 0	01	X 1
11	0 1	11	1 0	11	1 0
10	1 1	10	1 0	10	0 1

(2) D flip-flops

BA	C	0	1
00	X	0	0
01	0	1	1
11	0	1	1
10	1	1	1

(3) T flip-flop

BA	C	0	1
00	0	1	1
01	0	0	0
11	0	0	0
10	1	1	0

$$D_C = A'B + AC$$

$$T_C = A'C' + A'B'$$

(4) S-R flip-flop

(5) J-K flip-flop

BA	C	0	1
00	X	0	0
01	1	0	0
11	X	0	0
10	X	X	X

BA	C	0	1
00	X	X	X
01	0	X	X
11	0	1	1
10	0	0	0

BA	C	0	1
00	X	1	1
01	X	X	X
11	X	X	X
10	0	1	1

BA	C	0	1
00	X	X	X
01	0	1	1
11	1	0	0
10	X	X	X

$$S_B = B'C'$$

$$J_A = C$$

$$R_B = AC$$

$$K_A = B'C + BC'$$

2. (i)  $J_1 = X$

$K_1 = (XQ_2')'$

$J_2 = X$

$K_2 = (XQ_1)'$

$Z = X \oplus Q_2'$


$Q_1^+ = J_1 Q_1' + K_1' Q_1$

$= XQ_1' + XQ_1 Q_2'$

$Q_2^+ = J_2 Q_2' + K_2' Q_2$

$= XQ_2' + XQ_1 Q_2$

$Q_1 Q_2$	$Q_1^+ Q_2^+$		$Z$	
	$X=0$	$X=1$	$X=0$	$X=1$
00	00	11	1	0
01	00	10	0	1
10	00	11	1	0
11	00	01	0	1

 

3. (i) invalid BCD encoding: 1010, 1011, 1100, 1101, 1110, 1111


$\rightarrow 11xx, 101x$

$S_0$ : reset


$S_1$ : 1xxx

$S_2$ : 01xx



 

 
- (2)  $S_0 : 00XX$   
 $S_1 : 100X$   
 $S_2 : 01XX$   
 $S_3 : 11XX$  or  $101X$



4(1)

```
module mult_fast(  
    output reg[7:0] P, // product  
    input[3:0] A, B, // multiplicand and multiplier  
    input clk // clock (posedge)  
);  
    // stage 0 (input)  
    reg[3:0] a_s0, b_s0;  
    always @(posedge clk) begin  
        a_s0 <= A;  
        b_s0 <= B;  
    end  
    // stage 1  
    wire[3:0] pp0 = a_s0 & {4{b_s0[0]}}; // ignore the delays of AND gates  
    wire[4:1] pp1 = a_s0 & {4{b_s0[1]}}; // ignore the delays of AND gates  
    wire[5:2] pp2 = a_s0 & {4{b_s0[2]}}; // ignore the delays of AND gates  
    wire[6:3] pp3 = a_s0 & {4{b_s0[3]}}; // ignore the delays of AND gates  
    reg[5:1] sum1;  
    always @(pp0, pp1)  
        sum1[5:1] <= #7 pp0[3:1] + pp1[4:1]; // delay of the 4-bit adder  
    reg[7:3] sum3;  
    always @(pp2, pp3)  
        sum3[7:3] <= #7 pp2[5:3] + pp3[6:3]; // delay of the 4-bit adder  
    reg[5:0] sum1_s1;  
    reg[7:2] sum3_s1;  
    always @(posedge clk) begin  
        sum1_s1 <= {sum1, pp0[0]};  
        sum3_s1 <= {sum3, pp2[2]};  
    end  
    // stage 2 (outout)  
    reg[7:2] sum2;  
    always @(sum1_s1, sum3_s1)  
        sum2[7:2] <= #8 sum1_s1[5:2] + sum3_s1[7:2]; // delay of the 6-bit adder  
    always @(posedge clk) begin  
        P <= {sum2, sum1_s1[1:0]};  
    end  
endmodule
```


4(2)

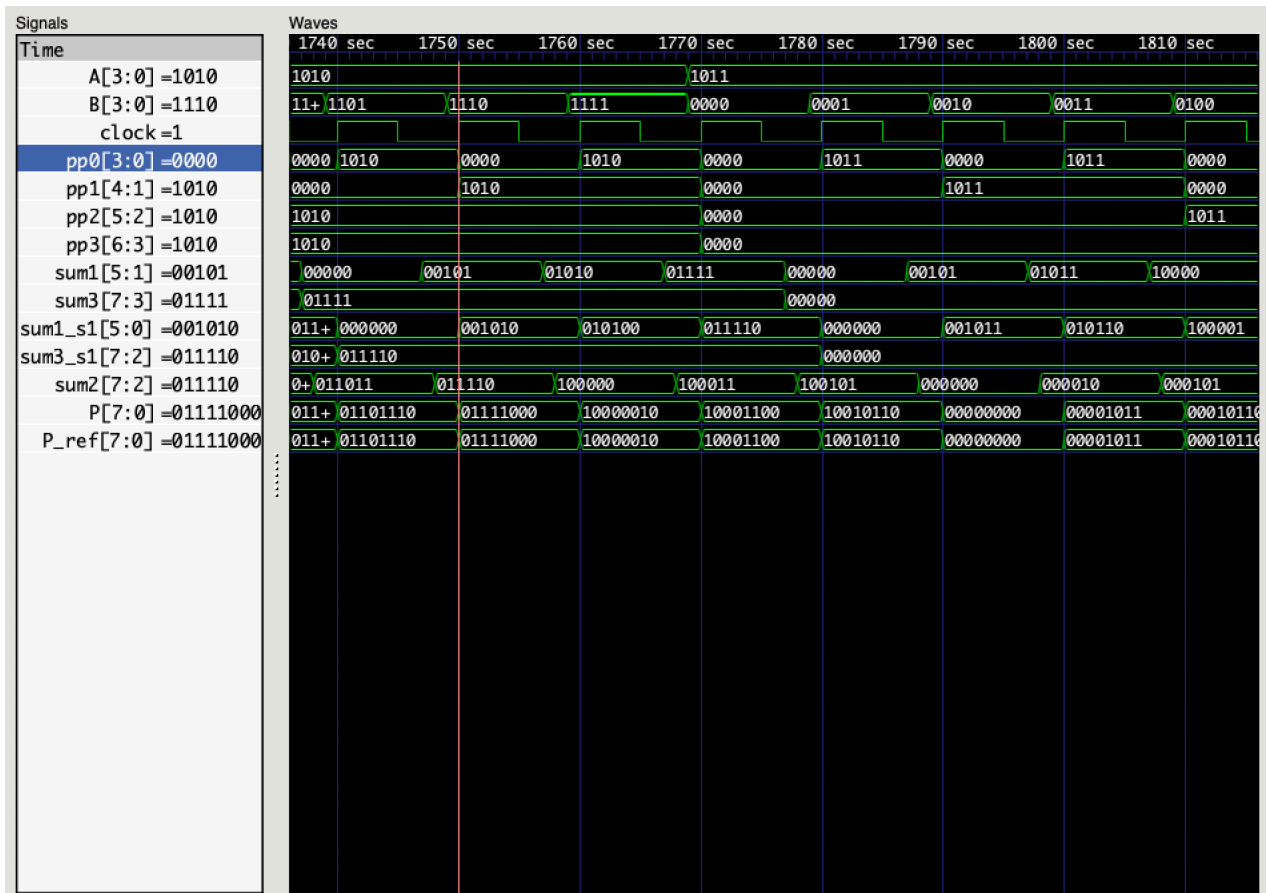

5(1)

The minimum clock cycle is 8 ticks.

5(2)

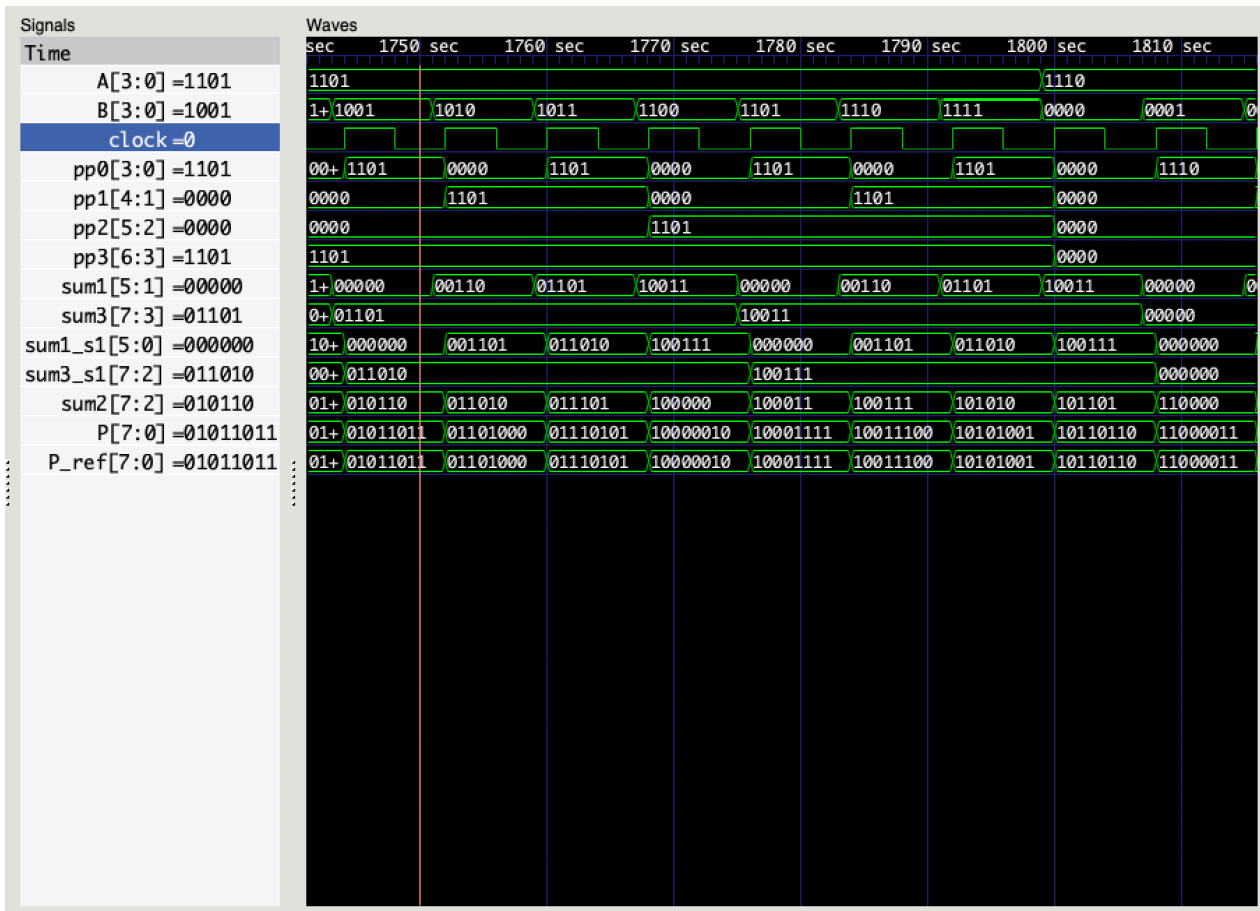

6(1)

Assume the clock cycle is 10 microseconds.

A logic operation can be done within 10 microseconds. That is to say  $\frac{1}{10 \times 10^{-6}} = 10^5$  logic operations can be done per second.

Therefore, the throughput is  $10^5$ .

6(2)

With the implementation of `mult_fast`, stage 0 can be done with no delay, stage 1 can be done with a delay of 7 microseconds, and stage 2 can be done with a delay of 8 microseconds.

Though stage 1 can be done with a delay of 7 microseconds, it still takes a clock cycle to move on to stage 2.

Therefore, the latency is  $10 + 8 = 18$  microseconds.